



Elementary Science

Simple Circuits

Level 2

Topic 10: Electricity & Magnets | Answer Sheet 2

Name: _____

Date: _____

A Match each circuit part to its job



battery

turns the circuit on or off



wire

changes electrical energy into light



bulb




provides electrical energy



switch

carries current around the circuit

B Which circuit lights the bulb?

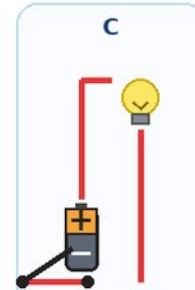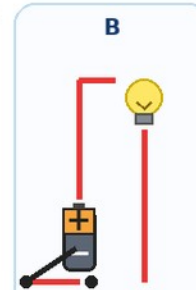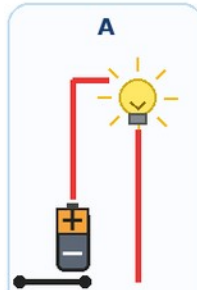

A complete, closed circuit lets current flow around the whole loop.

C Complete the sentences.

Word bank: battery wire bulb switch complete

1. The _____ provides electrical energy.
battery


2. A _____ carries current.
wire

3. A _____ can open or close a circuit.
switch

4. The _____ changes electrical energy into light.
bulb

5. The bulb lights only when the circuit is _____.
complete

D Challenge: Draw a complete circuit

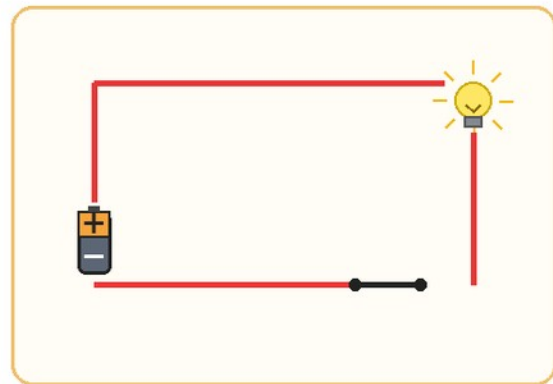

Use a battery, wires, a bulb and a closed switch.

A complete circuit makes a continuous path!